

1266432168421

University of Tripoli - Faculty of Engineering

Electrical & Electronic Engineering Department

EE463

Final Exam

Time: 2 hr

Spring 2017

3/2/2018

Q1) Temperature sensor sensitivity is $4\Omega/^\circ\text{C}$, in the range ($\pm 25^\circ\text{C}$) and its value at 0°C is 280Ω . Using Wheatstone bridge convert its range to volt, and send its value using (4mA - 20mA transmitter) and prepare it for 8bit ADC with voltage reference 0-5Vref.

a) What is the digital output of ADC at the temperature -2°C . [12 pts]

Q2) Accelerometer sensor sensitivity is 0.33mA/g used for measuring Acceleration in the range ($\pm 20\text{g}$). Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 4\text{V}$.

a) What is the digital output of ADC at the acceleration is -3g . [12

b) What is the acceleration when the digital output is 06H. [12 pts]

Q3) Design the signal conditioning circuits to connect the sensor to 10 bit ADC with voltage reference (0-5V), where: sensor output range ($-150 - +150\text{mV}$) with frequency 15Hz. Noise signal 20mV with frequency 150Hz, and design filter that Attenuate the noise signal to 25%, and taking in account the effect of the filter on the sensor signal. [10 pts]

$V_s = 17.68\text{mV}$

Q4) Using Thermocouple sensor Type J with 0°C reference, find the value of its output at 32°C . Design circuit to operate cooler if the temperature is more than 32°C , and using RTD with the following table using linear approximation of resistance versus temperature find the value of the RTD at 13°C and design circuit operate heater if the temperature is less than 13°C . [12 pts]

Temperature ($^\circ\text{C}$)	0	5	10	15	20
Resistance (Ω)	107.6	109.1	110.2	111.1	111.7

RTD: 110.2Ω
 $V_{in} = 1.936\text{mV}$

Q5) What is the sampling and sample and hold and aliasing and oversampling (Draw as you can). [4 pts]

Good Luck (Zeyad)

Q4) Thermocouple Sensor Type J with 0°C ref
 o/p if $T = 32^\circ\text{C}$ to operate collar ~~at 32°C~~ $T > 32^\circ\text{C}$
 using RTD with Table using linear approximation
 RTD ? at 13°C
 - operate heater if $T < 13^\circ\text{C}$

T	0	5	10	15	20
R	107	109.4	110.2	111.1	111.5

$$V_L = 1.54 \text{ mV} \quad T_L = 30^\circ$$


$$V_H = 1.80 \text{ mV} \quad T_H = 35^\circ$$

$$T_m = 32^\circ\text{C}$$

$$V_m = V_L + \left[\frac{V_H - V_L}{T_H - T_L} \right] (T_m - T_L)$$

$$= 1.54 + \left[\frac{1.80 - 1.54}{35 - 30} \right] (32 - 30)$$

$$V_m = 1.644$$

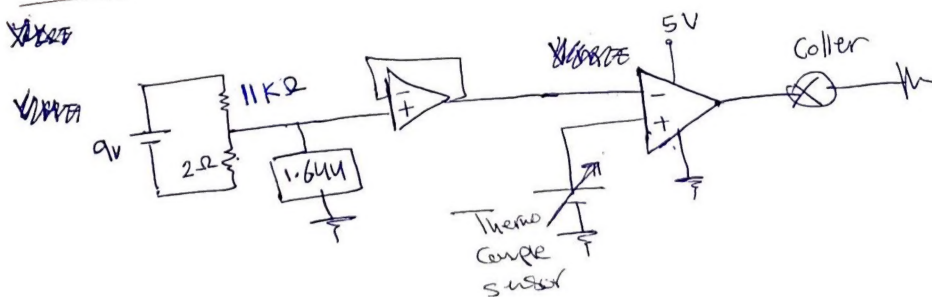

$$Q \times \frac{R}{11K\Omega + R} = 1.644 \text{ mV}$$

$$R = 2.5 \Omega \#$$

$$T_1 = 0, R_1 = 107$$

$$T_0 = 10, R_0 = 110.2$$

$$T_2 = 20, R_2 = 111.5$$

$$\alpha_0 = \frac{1}{R(T_0)} \times \frac{R_2 - R_1}{T_2 - T_1} = \frac{1}{110.2} \times \frac{111.5 - 107}{20 - 0} = 2.041 \times 10^{-3}$$

$$R(T) = R(T_0) (1 + \alpha_0 \Delta T)$$

$$= 110.2 [1 + 2.041 (13 - 10)]$$

$$= 110.87 \Omega$$

